

Correction du TD 3 VHDL

Correction Exercise 1 :

```

Entity ex01 is port (
    BP: in std_logic (5 DOWN TO 0);
    RST: in std_logic;
    LED: out std_logic (5 DOWN TO 0);
end ex01;

ARCHITECTURE And of ex01 is
    Signal s_g: std_logic_vector (5 DOWN TO 0);
begin
    LED <= s_g;
    Process BP, RST
    wait on BP, RST;
    if RST = '1' then s_g = "000000";
    else s_g <= BP;
    end if;
end Process;
end And;
  
```

Correction Exercise 2 :

```

ARCHITECTURE RUNLIFT for LIFT IS
    SIGNAL COMPTEUR, UNSIGNED (0 to 5) <= "0000";
begin
    Comptage process
    begin
        Wait until CLK = '1';
        If (RST = '1') then
            COMPTEUR <= "0000";
        elsif (UP = '1') then
            Case COMPTEUR IS
                When "0000" => COMPTEUR <= COMPTEUR;
                When "1000" => COMPTEUR <= "1000";
                When others => COMPTEUR <= COMPTEUR + 1;
            End Case;
        elsif (DN = '1') then
            Case COMPTEUR IS
                When "0000" => COMPTEUR <= COMPTEUR;
                When "1000" => COMPTEUR <= "1000";
                When others => COMPTEUR <= COMPTEUR - 1;
            End Case;
        end if;
    end process;
end RUNLIFT;
  
```


Correction du TD 4 VHDL

Correction Exercice 1 :

```
Library ieee;  
use ieee.std_logic_1164.all;  
entity compareur8bits is port  
    (A, B: in std_logic_vector (7 downto 0);  
     EQUA, SUPE, INFE: out std_logic);  
end compareur8bits;  
  
architecture ARCH_compareur8bits of compareur8bits is  
Begin  
    EQUA<='1' when A=B else '0';  
    SUPE<='1' when A>B else '0';  
    INFE<='1' when A<B else '0';  
end ARCH_compareur8bits;
```

Correction Exercice 2 :

1- Le schéma correspondant

 

2- C'est une description comportementale, puisqu'il n'y a aucune composante.

C'est un processus combinatoire car il inclut toutes les entrées (signaux lus) dans la liste de sensibilité. De plus, toutes les valeurs possibles de sel sont traitées.

3 - C'est un plein additionneur avec multiplexage des sorties somme et retenue.

4- architecture archi2 of exercice2 is

```
signal a, b, c, d, e, f: std_ulogic;  
signal ytemp: std_logic;  
begin  
    a <= x1 or x3;
```

```

b <= x1 and x3;
c <= x2 and a;
d <= b or c;
e <= x1 xor x2;
f <= x3 xor e;
P1: process (d, f, sel)
begin
if sel='0' then
ytemp <= d;
else
ytemp <= 'z';
end if;
end process P1;
P2: process (d, f, sel)
begin
if sel='1' then
ytemp <= f;
else
ytemp <= 'z';
end if;
end process P2;
y <= ytemp;
end architecture archi;

```

Correction Exercise 3 :

```

Library ieee;
use ieee.std_logic_1164.all;
-- entity statement
Entity Moore_Machine is port
(x, CLK : in BIT; S1,S2 : out BIT);
End Moore_Machine;
-- architecture statement

```

```

Architecture FSM of Moore_Machine is
type STATE_TYPE is (Etat0, Etat1, Etat2, Etat3);
signal STATE : STATE_TYPE := Etat0;
signal S :bit_vector (1 downto 0);
begin
--block funtion
NEXT_STATE: block (CLK'event and CLK='1')
begin
-- guarded conditional concurrent signal assignment statement
STATE <= guarded Etat0 when (STATE=Etat0 and x='0') else
    Etat1 when (STATE=Etat0 and x='1') else
    Etat2 when (STATE=Etat1 and x='1') else
    Etat3 when (STATE=Etat2 and x='0') else
    Etat2 when (STATE=Etat2 and x='1') else
    Etat0 when (STATE=Etat3 and x='0') else
    Etat1 when (STATE=Etat3 and x='1') else

```

```

        Etat3 when (STATE=Etat1 and x='0') else
        STATE;
end block NEXT_STATE;
-- unguarded selected concurrent signal assignment statement

```

```

with STATE select
S <= "00" when Etat0,
  "10" when Etat1,
  "11" when Etat2,
  "01" when Etat3,
  "00" when others;

```

```

S1<=S(0);
S2<=S(1);
End FSM;

```

```

library ieee;
use ieee.std_logic_1164.all;

--library SYNTH ;
--use SYNTH.vhdlsynth.all ;

```

----- Définition de l'entité-----

```

ENTITY diagramme IS
PORT (raz, clk :IN STD_LOGIC; -- Ne pas oublier remise à 0 et horloge !
      x :IN bit;
      S1,S2 :OUT STD_LOGIC);
END diagramme;

```

----- Définir L'architecture de description d'état -----

```

ARCHITECTURE arch_diagramme OF diagramme IS
  TYPE etat_4 IS (A, B, C, D); --définir une liste des états...
  SIGNAL etat,etat_suiv :etat_4 := A; --et 2 signaux: états courant et --suivant,
  contenant la valeur d'un état de la liste (initialisée à M0) .
  signal S :std_logic_vector (1 downto 0);
BEGIN
  definir_etat:PROCESS( raz, clk) -- "definir_etat":label optionnel
  BEGIN
    If raz = '1' THEN
      etat <= A; --Le PACKAGE std_logic_1164
    ELSIF rising_edge(clk) THEN --en permet l'utilisation.
      etat <= etat_suiv ;
    END IF; --Mise à jour de la
variable
  END PROCESS definir_etat;

```

----- Définir les états des sorties-----

sorties : process (etat, x) --Le PROCESS doit contenir une...
 BEGIN --structure de CAS unique
dépendant --de la variable d'état.

CASE etat IS
--Le signal de l'état suivant n'est
--attribué que dans la structure CASE

WHEN A => S <= "00";

If x='1' then etat_suiv <= B;
elsif x='0' then etat_suiv <= A;
end if;

WHEN B => S <= "10";

If x='1' then etat_suiv <= C;
elsif x='0' then etat_suiv <= D;
end if;

WHEN C => S <= "11";

If x='1' then etat_suiv <= C;
elsif x='0' then etat_suiv <= D;
end if;

WHEN D => S <= "01";

If x='1' then etat_suiv <= B;
elsif x='0' then etat_suiv <= A;
end if;


END CASE;

END process sorties ;

S1<=S(0);

S2<=S(1);

 END arch_diagramme ; -- ne pas oublier de terminer l'architecture !



Correction Exercice 5 :

```
library ieee ;
use ieee.std_logic_1164.ALL;

entity MAE is          --MAE = Machine A Etat
  port ( E,RST,HOR      : in  STD_LOGIC ;
         S              : out STD_LOGIC );
end MAE;

architecture COMPOTEMENT of MAE is
  signal REG_ETAT      : STD_LOGIC_VECTOR(2 downto 0);
  process (HOR,RST)
  begin
    if RST='0' then REG_ETAT <= "000";
      elsif (HOR'event and HOR='1') then
        case REG_ETAT is
          when "000" => S = '0' ;
                        if E = '1' then REG_ETAT <= "001";
                        else REG_ETAT <= "000";
                        end if ;
          when "001" => S = '0' ;
                        if E = '1' then REG_ETAT <= "010";
                        else REG_ETAT <= "000";
                        end if ;
          when "010" => S = '0' ;
                        if E = '1' then REG_ETAT <= "011";
                        else REG_ETAT <= "000";
                        end if ;
          when "011" => S = '1' ;
                        if E = '1' then REG_ETAT <= "011";
                        else REG_ETAT <= "100";
                        end if ;
          when "100" => S = '1' ;
                        if E = '1' then REG_ETAT <= "011";
                        else REG_ETAT <= "101";
                        end if ;
          when "101" => S = '0' ;
                        if E = '1' then REG_ETAT <= "011";
                        else REG_ETAT <= "000";
                        end if ;
          when others => REG_ETAT <= "00";
        end case ;
      end if ;
    end process ;
  end COMPOTEMENT ;
```